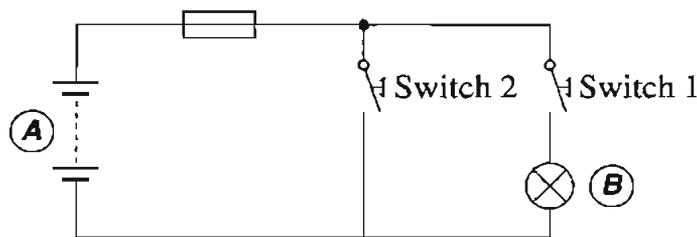


Electrotechnology

Section II (continued)

Question 19 (7 marks)

An electrical circuit is shown.



- (a) Identify the components (A) and (B).

	Component	
(i)	(A) Power Supply	1
(ii)	(B) Globe	1

- (b) Describe what will happen if Switch 1 is closed. 2

If switch one is closed the globe (called B) will light up as the circuit is complete.

- (c) Describe what will happen if Switch 1 remains closed and Switch 2 is also closed. 3

If switch 2 is closed the globe will go out because the switches are in parallel making the globe function regardless as long as they are turned opposite.