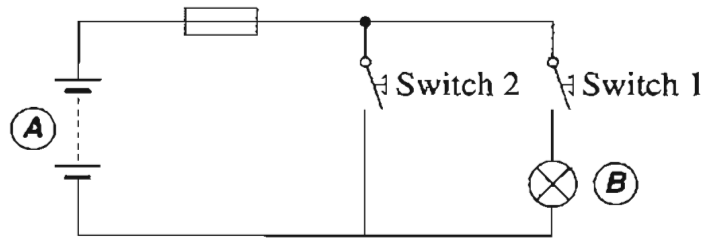


Electrotechnology

Section II (continued)

Question 19 (7 marks)

An electrical circuit is shown.



- (a) Identify the components **(A)** and **(B)**.

		Component	
(i)	(A)	Battery	1
(ii)	(B)	Lamp	1

- (b) Describe what will happen if Switch 1 is closed.

The current will pass through the lamp and the lamp will operate. As current will always take the easiest path

- (c) Describe what will happen if Switch 1 remains closed and Switch 2 is also closed.

The current will take the easiest path therefore the lamp will not turn on and the circuit will now be shorting.