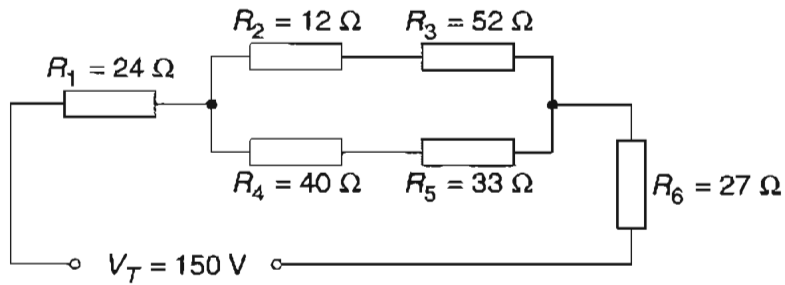


**Question 24** (3 marks)

Calculate the total resistance of the electrical circuit shown. Show all your working in the space provided.

3



$$12 + 52 = 64$$

$$40 + 33 = 73$$

$$24 + 34.1 + 27 = 55.1 \Omega$$

$$\frac{1}{\frac{1}{64} + \frac{1}{73}} = 34.1$$

$$R_T = 55.1 \Omega$$

